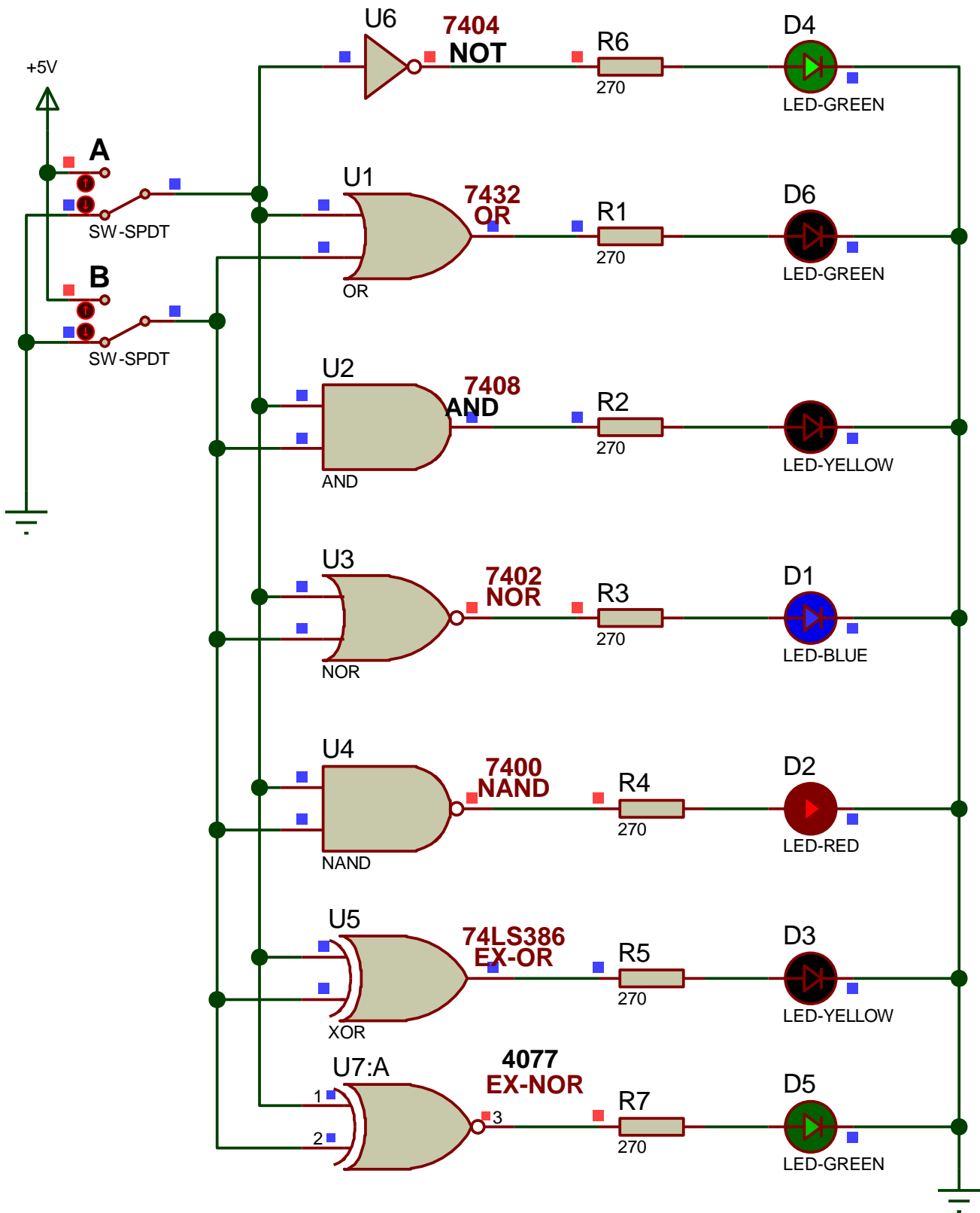


VERIFICA TAVOLE DI VERITA' PORTE LOGICHE ELEMENTARI


A	NOT $Y = \bar{A}$
0	1
1	0

A	B	OR $Y = A+B$	NOR $Y = \overline{A+B}$	AND $Y = A*B$	NAND $Y = \overline{A*B}$	EX-OR $Y = \bar{A}B + A\bar{B}$	EX-NOR $Y = \bar{\bar{A}}\bar{\bar{B}} + \bar{\bar{A}}\bar{\bar{B}}$
0	0	0	1	0	1	0	1
0	1	1	0	0	1	1	0
1	0	1	0	0	1	1	0
1	1	1	0	1	0	0	1


1° CASO : A B = 0 0



2° CASO : A B = 0 1

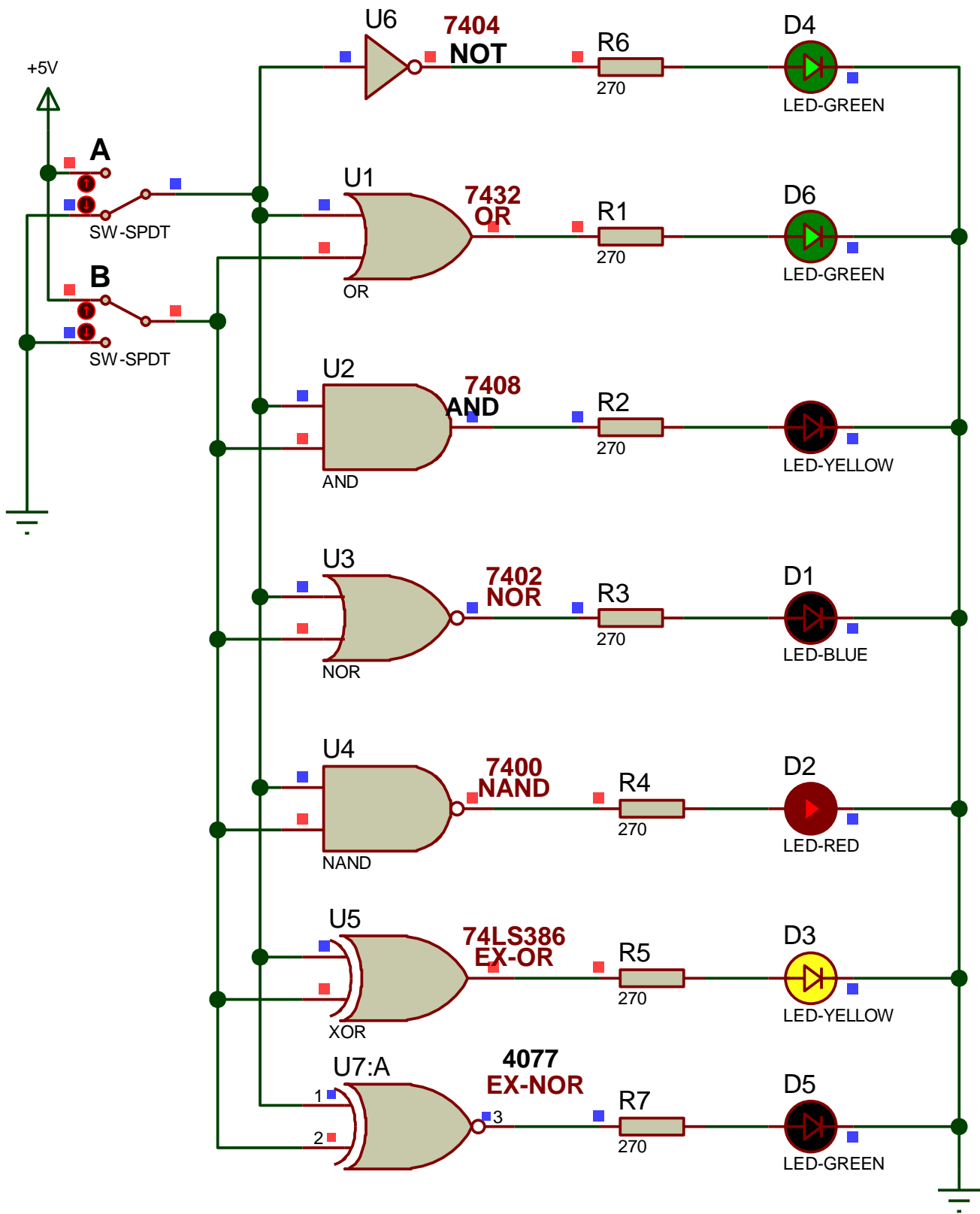

3° CASO : A B = 1 0

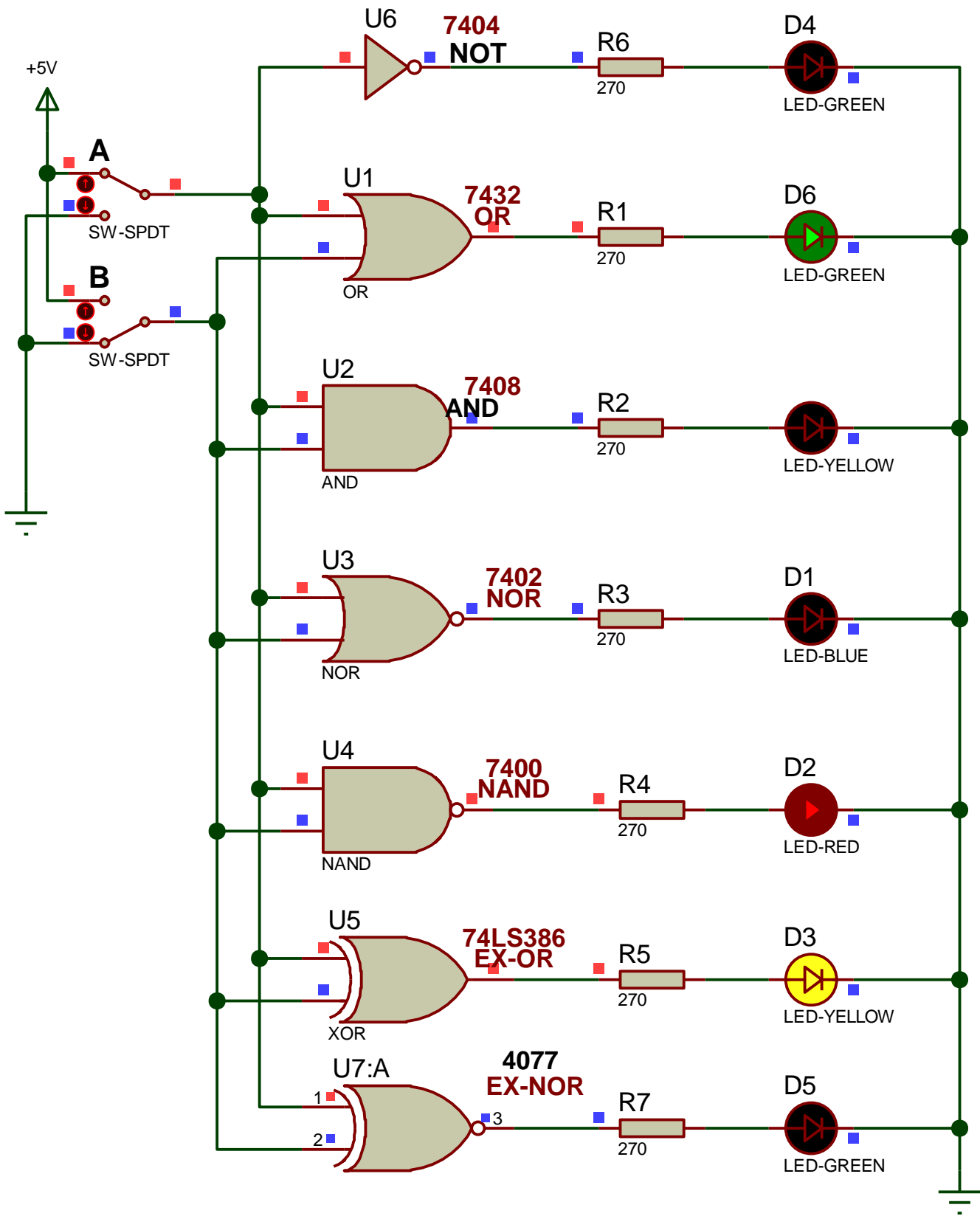

4° CASO : A B = 1 1

