
 

 
# INTEGRATI TTL

Quadruple  
2 - input  
positive  
NAND gates  
**00**




 Quadruple  
2 - input  
positive - NOR  
gates  
**02**

 


**Fig. 106**  
Piedinature di  
alcuni circuiti  
integrati SSI della  
serie digitale 74  
(tensione di  
alimentazione  
 $+5\text{ V} \pm 5\%$ ).


Hex inverters  
**04**




Quadruple  
2 - input  
positive  
AND gates  
**08**



 
Quadruple  
2 - input positive  
AND gates with  
open collector  
outputs  
**09**




Triple  
3 - input  
positive  
NAND gates  
**10**

 

 
Triple 3 - input  
positive NAND  
gates with open-  
collector outputs  
**12**




Hex  
Schmitt-Trigger  
inverters  
**14**

 

 
Triple 3 - input  
positive AND gates  
with open-collector  
outputs  
**15**



 
Hex inverter  
buffers/drivers  
with open collector  
high-voltage  
output  
**16**



 
Hex buffers /  
drivers with open -  
collector high-  
voltage outputs  
**17**



 
Quadruple  
2 - input  
high-voltage  
positive - NAND  
gates  
**26**



 
Triple  
3 - input  
positive - NOR  
gates  
**27**



 
Quadruple  
2 - input  
positive - NOR  
buffers  
**28**



 
Quadruple  
2 - input  
positive - OR  
gates  
**32**



 Quadruple  
2 - input  
exclusive - OR  
gates  
**86**



 Quadruple  
2 - input  
positive  
NAND gates  
**00**



Quadruple  
2 - input  
positive - NOR  
gates  
**02**

