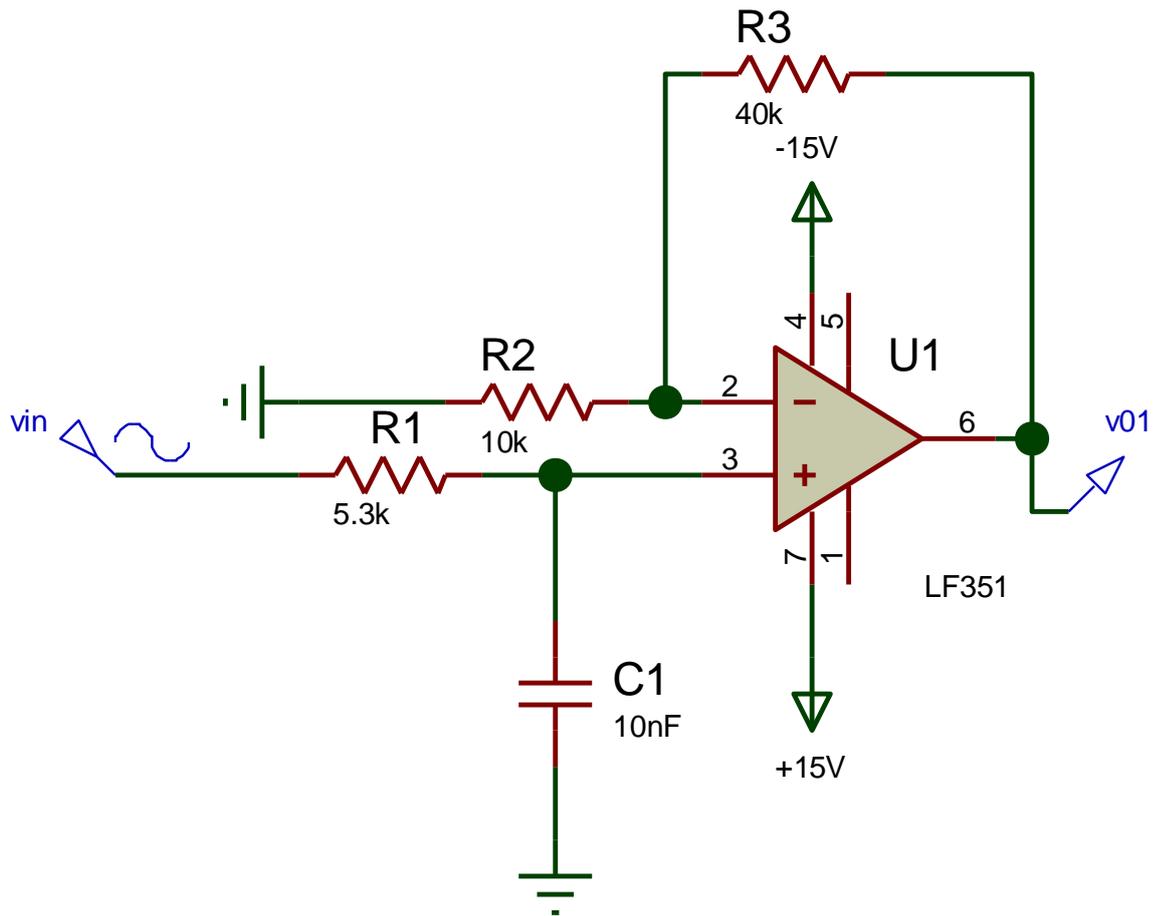


2) Filtro attivo RC Passa Basso NON invertente del 1° ordine : disegnare lo schema e dimensionare i componenti in modo che $G_{LF} = 14$ [dB] , $f_t = 3000$ [Hz]

a)



$$f_t = 3000 \text{ [Hz]} \quad \text{pongo} \quad C_1 = 10 \text{ [nF]} \quad \ggggg \quad R_1 = 1 / (2\pi \cdot 3.000 \cdot 10^{-8}) = 5,3 \text{ [K}\Omega\text{]}$$

$$G_{LF} = 14 \text{ [dB]} \quad \ggggg \quad |V_{out} / V_{in}| = 5 \quad \text{essendo} \quad G_{LF} = 1 + R_3/R_2$$

$$\text{pongo} \quad R_2 = 10 \text{ [K}\Omega\text{]} \quad \ggggg \quad R_3 = 40 \text{ [K}\Omega\text{]}$$

$$\text{b) } G(j\omega) = \frac{1 + R_3 / R_2}{1 + j\omega R_1 C_1}$$