
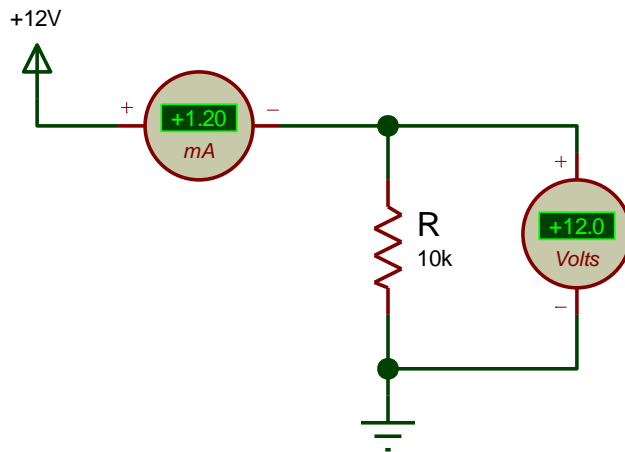


CIRCUITI ANALOGICI RESISTIVI

1. CIRCUITI SERIE – Legge di Ohm

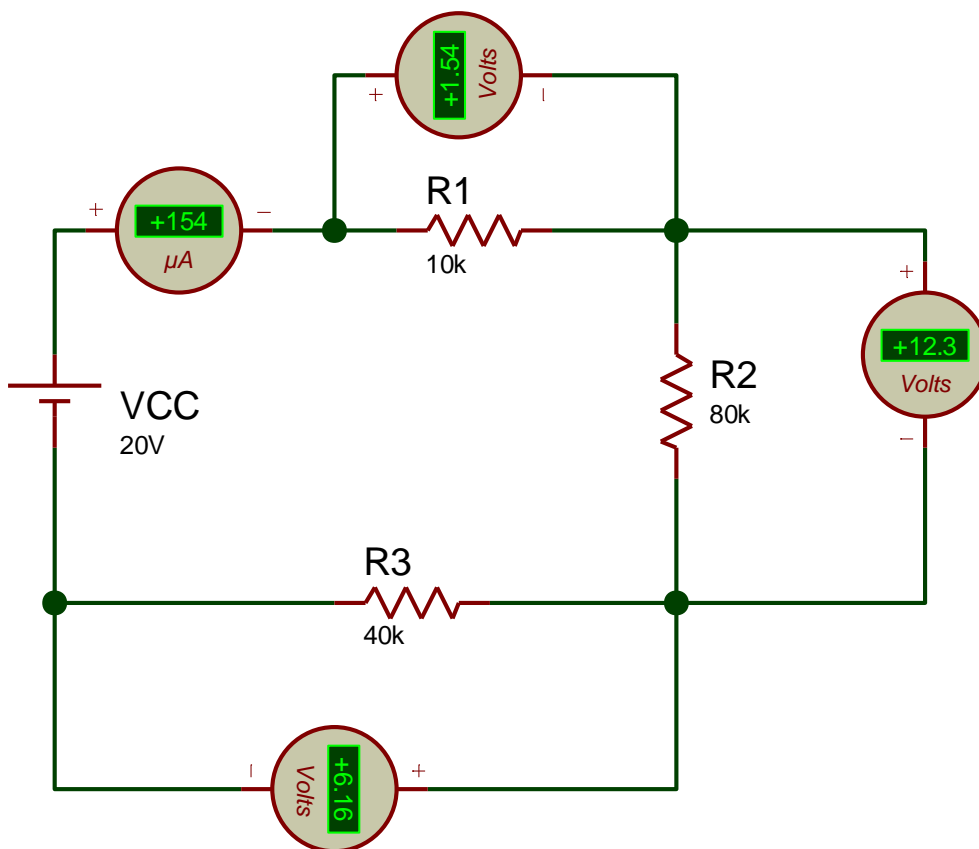

LEGGE di OHM : $V = R * I$ $I = V/R$ $R = V/I$



$$R_{eq} = R1 + R2 + R3 = 130 \text{ [KOhm]}$$

$$I = V_{cc} / R_{eq} = 20 / 130 = 0,15 \text{ [mA]}$$


$$V_{R1} = I * R1 = 1,54 \text{ [V]}$$

$$V_{R2} = I * R2 = 12,3 \text{ [V]}$$

$$V_{R3} = I * R3 = 6,16 \text{ [V]}$$

$$V_{R1} = V_{cc} * R1 / R_{eq}$$

2. PARTITORE DI TENSIONE

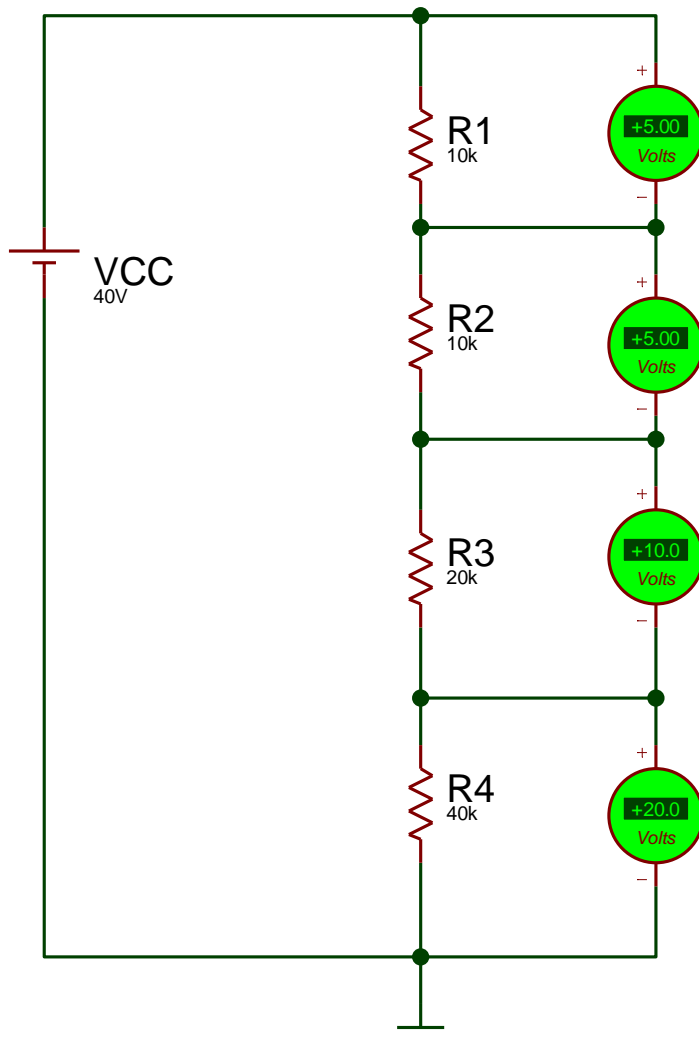


$$VR1 = 40 * 10 / (40+20+10+10) = 5 [V]$$

$$VR2 = 40 * 10 / (40+20+10+10) = 5 [V]$$

$$VR3 = 40 * 20 / (40+20+10+10) = 10 [V]$$

$$VR4 = 40 * 40 / (40+20+10+10) = 20 [V]$$

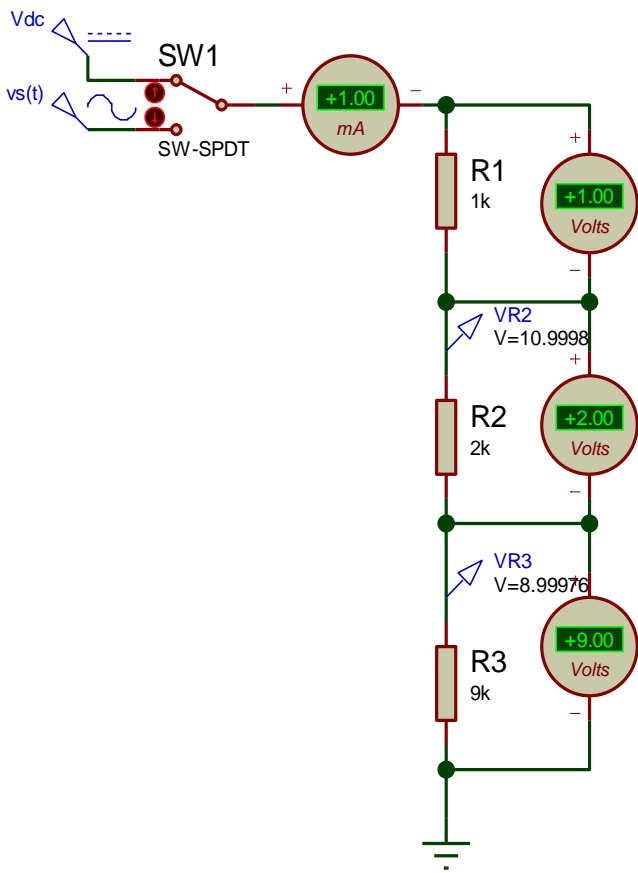3. PARTITORE DI TENSIONE IN DC E IN REGIME SINUSOIDALE




$$R_{eq} = R1 + R2 + R3 = 12 \text{ k}$$

$$VR1 = Vg * R1 / R_{eq} = 12 * 1 / 12 = 1 \text{ [V]}$$


$$VR2 = Vg * R2 / R_{eq} = 12 * 2 / 12 = 2 \text{ [V]}$$

$$VR3 = Vg * R3 / R_{eq} = 12 * 9 / 12 = 9 \text{ [V]}$$
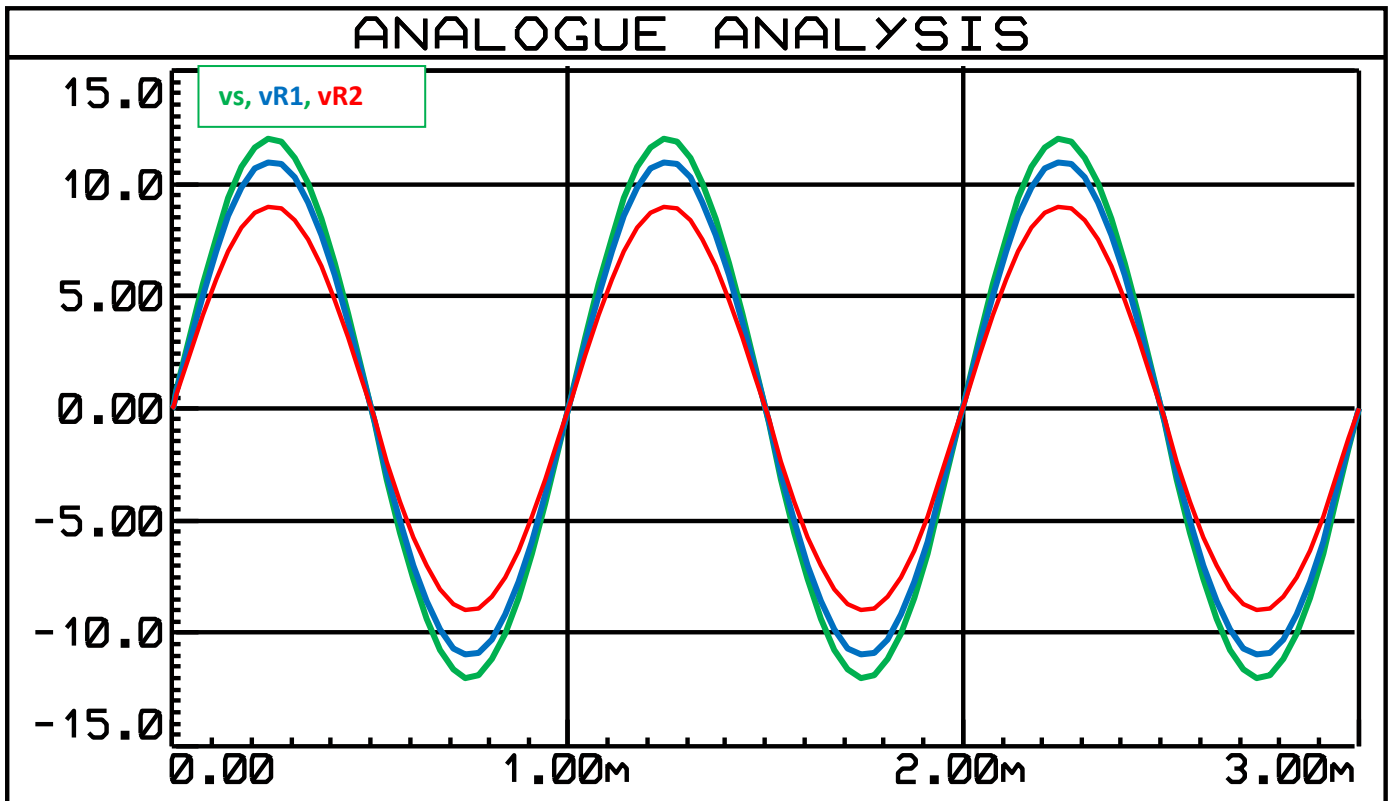
$$I_g = Vg / R_{eq} = 12 / 12 = 1 \text{ [mA]}$$



4. CIRCUITO SERIE – PARALLELO 1

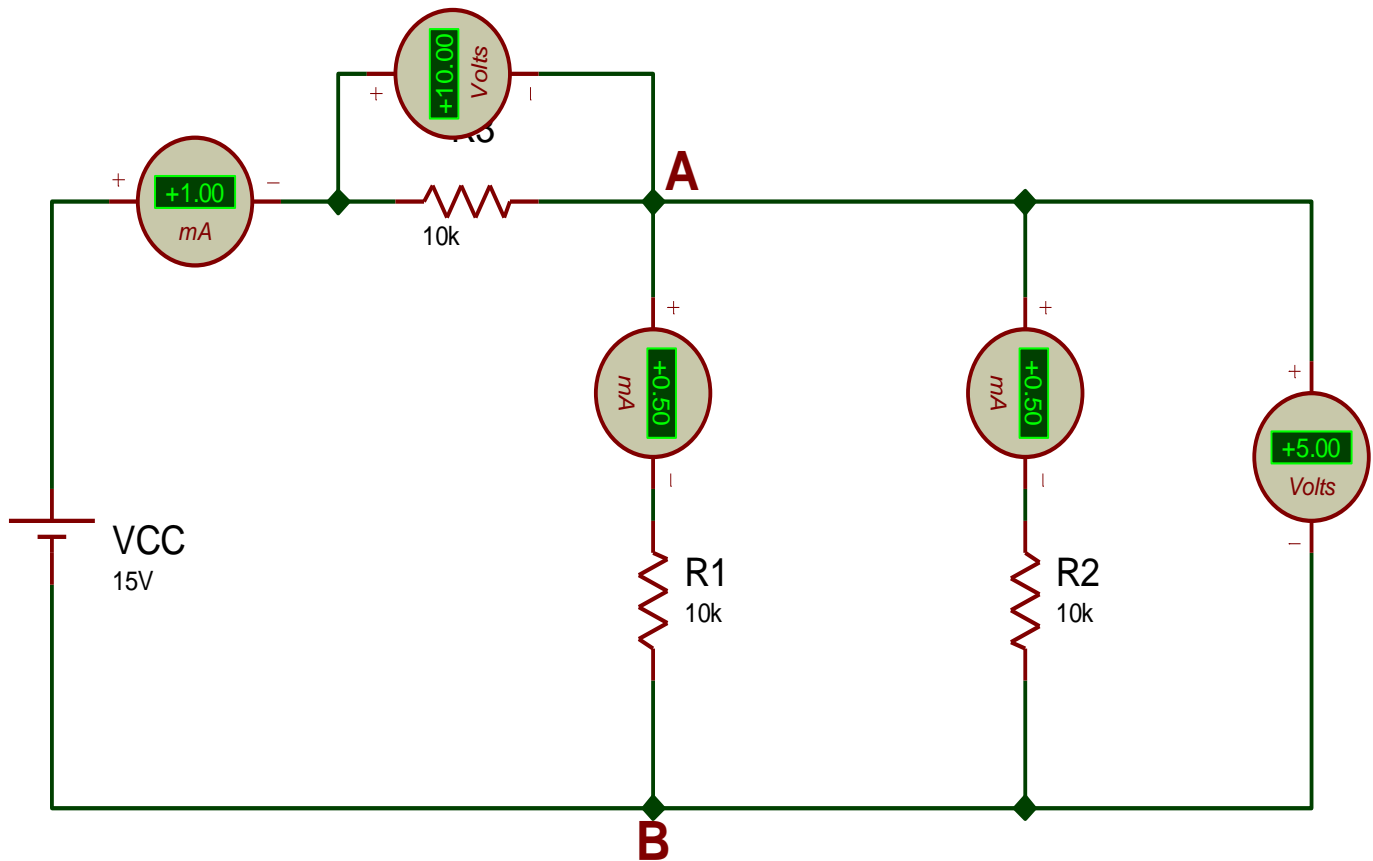


$$R_{eq} = R_3 + (R_1 // R_2) = R_3 + R_p = 10 + (10 // 10) = 15 \text{ [KOhm]}$$

$$V_{AB} = V_{cc} * R_{AB} / R_{eq} = V_{cc} * (R_1 // R_2) / [R_3 + (R_1 // R_2)] = 15 * 5 / 15 = 5 \text{ [V]}$$

$$I_{cc} = V_{cc} / R_{eq} = 15 / 15 = 1 \text{ [mA]}$$

$$I_{R1} = I_{R2} = I_{cc} / 2 = 0,5 \text{ [mA]}$$

4. CIRCUITO SERIE – PARALLELO 2

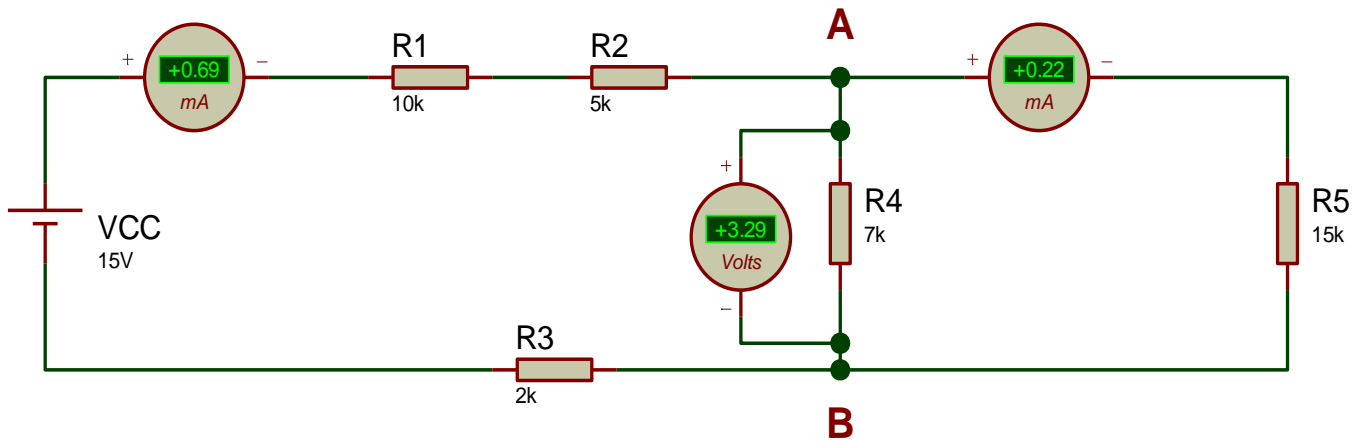

$$R_{eq} = 10 + 5 + (7 // 15) + 2 = 10 + 5 + 4.8 + 2 = 21.8k$$

$$I_{r5} = I_{cc} - I_{r4} = 0.69 - 0.47 = 0.22 \text{ [mA]}$$


$$I_{cc} = V_{cc} / R_{eq} = 15 / 21.8 = 0.69 \text{ [mA]}$$

$$V_{ab} = I_{cc} * R_{p1} = 0.69 * 4.8 = 3.31 \text{ [V]}$$

$$V_{ab} = V_{cc} * R_{p1} / R_{eq} = 15 * 4.8 / 21.8 = 3.30 \text{ [V]}$$

$$I_{r4} = V_{ab} / R_4 = 3.31 / 7 = 0.47 \text{ [mA]}$$

5. CIRCUITO SERIE – PARALLELO 3

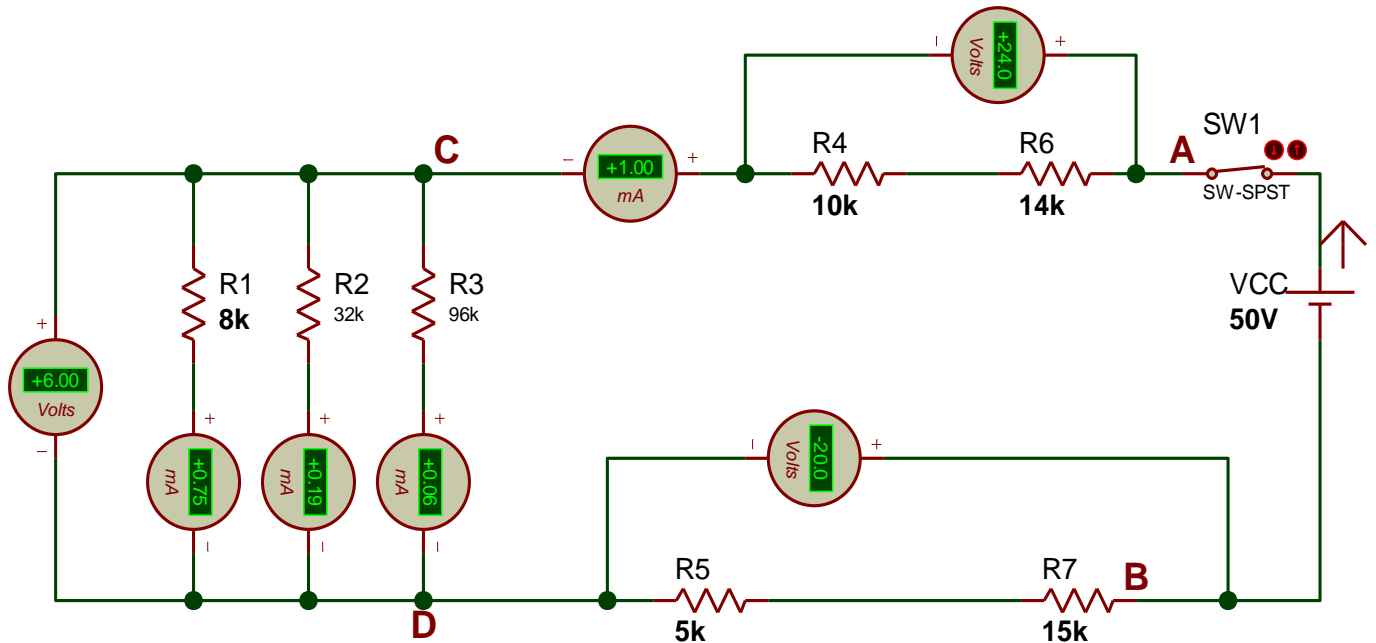

1) $R_{AB} = 14 + 10 + 6 + 5 + 15 = 50 \text{ K}$

2) $I_{cc} = V_{cc} / R_{eq} = 50 / 50 = 1 \text{ [mA]}$


3) $V_{CD} = I_{cc} * R_P = 1 * 6 = 6 \text{ [V]}$

4) $I_{R1} = V_{CD} / R1 = 6 / 8 = 0,75 \text{ [mA]}$ $I_{R2} = 6 / 32 = 0,1875 \text{ [mA]}$ $I_{R3} = 6 / 96 = 0,0625 \text{ [mA]}$

5) $V_{CD} = V_{cc} * R_P / R_{EQ} = 50 * 6 / 50 = 6 \text{ [V]}$

6) $V_{CD} = V_{cc} - (R4 + R5 + R6 + R7) * I_{cc} = 50 - 44 * 1 = 6 \text{ [V]}$

6. CIRCUITO SERIE – PARALLELO 4

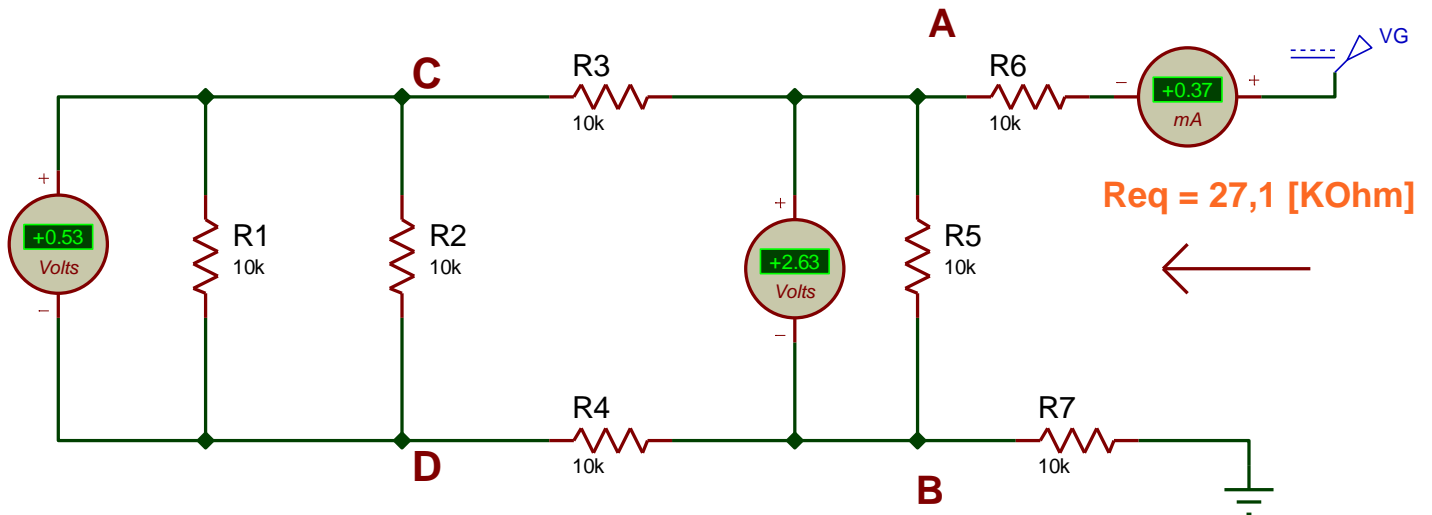


$$R_{eq} = [(R1 // R2 + R3 + R4) // R5] + R6 + R7 = [(5 + 10 + 10) // 10] + 10 + 10 = 27,1 [KOhm]$$

$$R_{AB} = (10 // 10 + 10 + 10) // 10 = 25 // 10 = 7,14 K$$


$$V_{AB} = V_g * R_{AB} / R_{eq} = 10 * 7,14 / 27,1 = 2,63 [V]$$

$$V_{CD}(t) = 2,63 * 5 / 25 = 0,53 [V]$$

7. CIRCUITO SERIE – PARALLELO 5

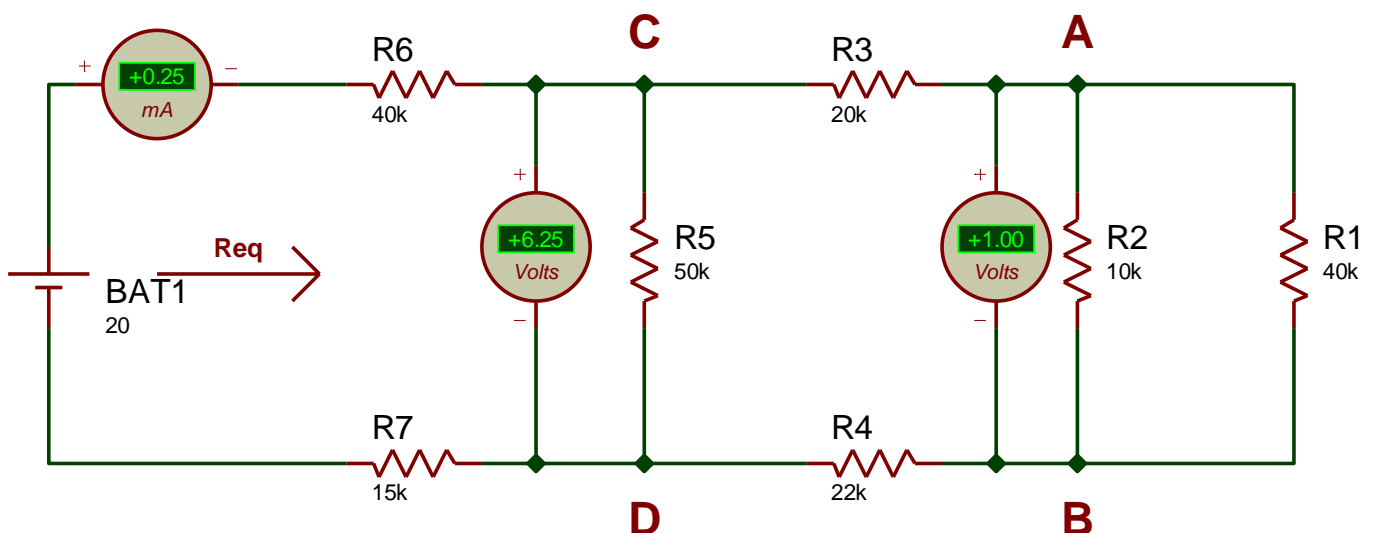

8. CIRCUITO SERIE – PARALLELO 6

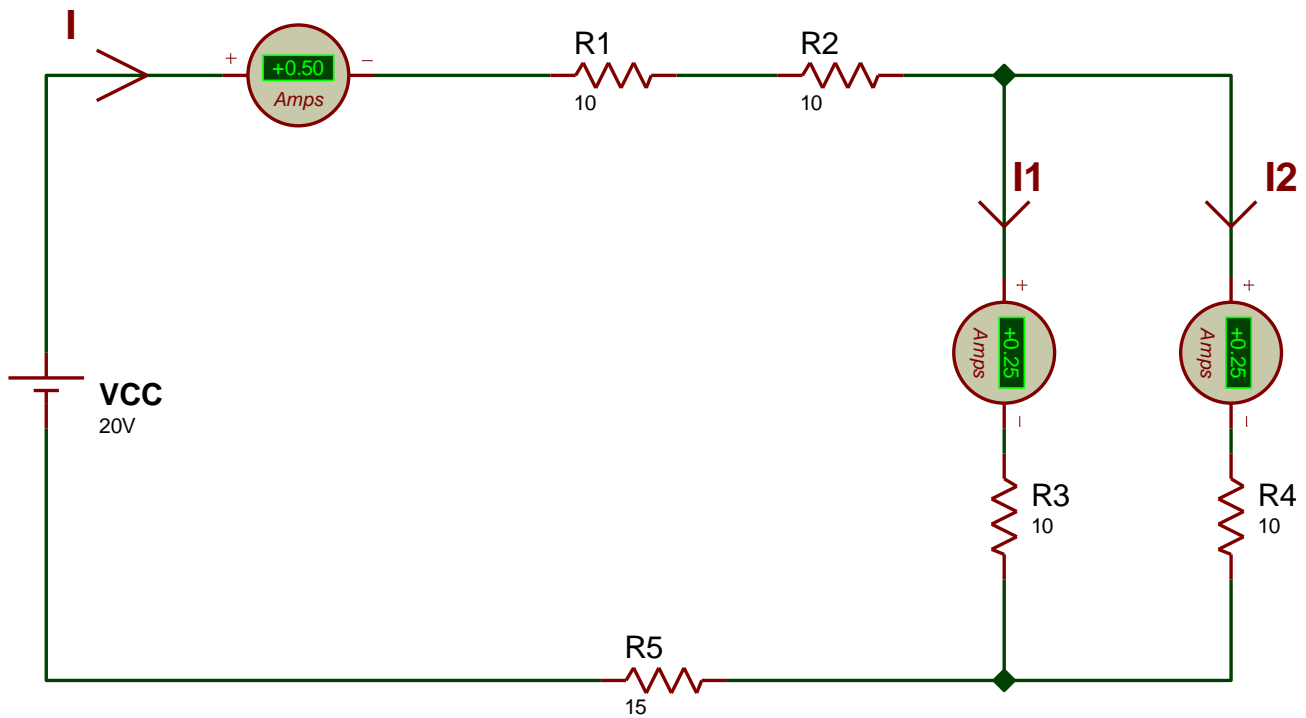


$$R_{eq} = 10 + 10 + \left[\frac{10 \cdot 10}{10 + 10} \right] + 15 = 40 \text{ [Ohm]}$$

$$I = V_{cc} / R_{eq} = 20 / 40 = 0.5 \text{ [A]}$$

$$I_1 = I_2 = I_{cc} / 2 = 0,25 \text{ [mA]}$$

9. CIRCUITO SERIE – PARALLELO 7

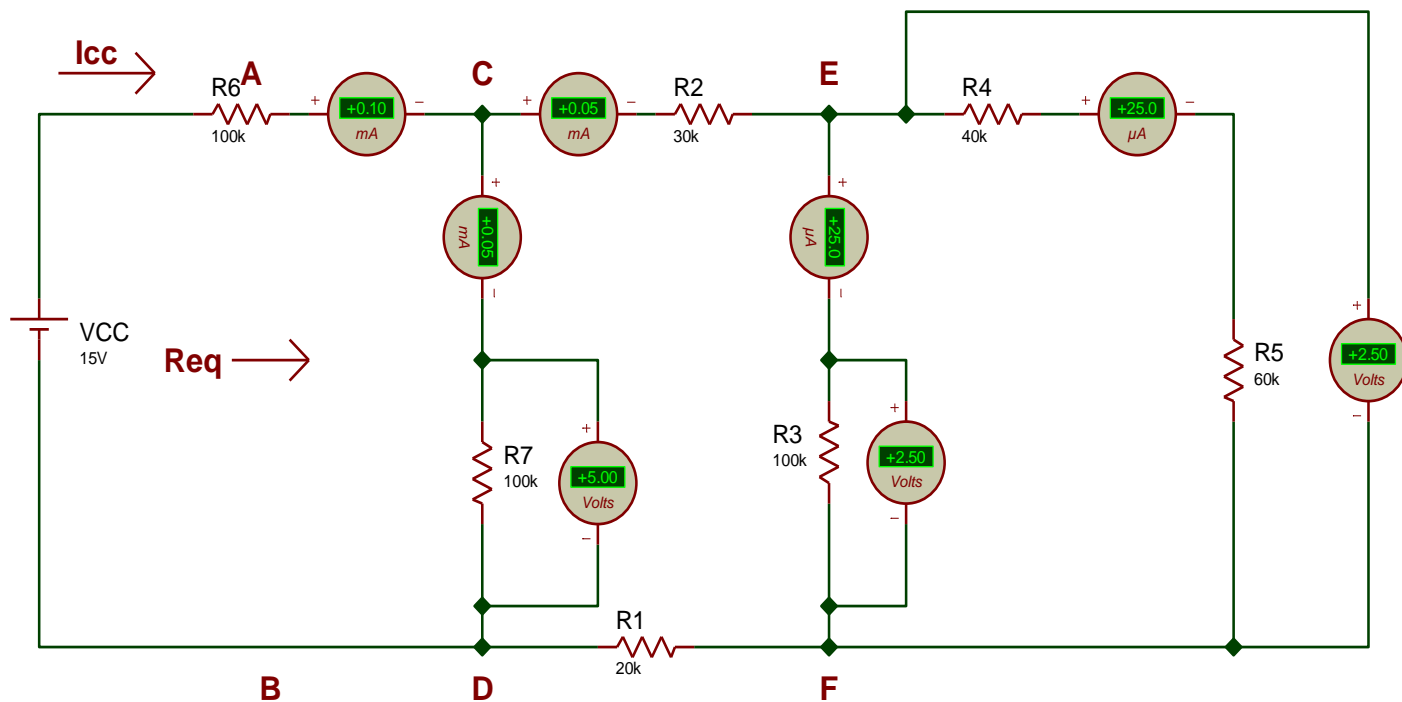

$Req = 150 \text{ [Ohm]}$

$Rcd = 50 \text{ [Ohm]}$


$Ref = 50 \text{ [Ohm]}$

$Vcd = Vcc * Rcd / Req = 15 * 50 / 150 = 5 \text{ [V]}$


$Vef = 5 * 50 / 100 = 2,5 \text{ [V]}$

10. ACCENSIONE 3 LED IN PARALLELO


a)

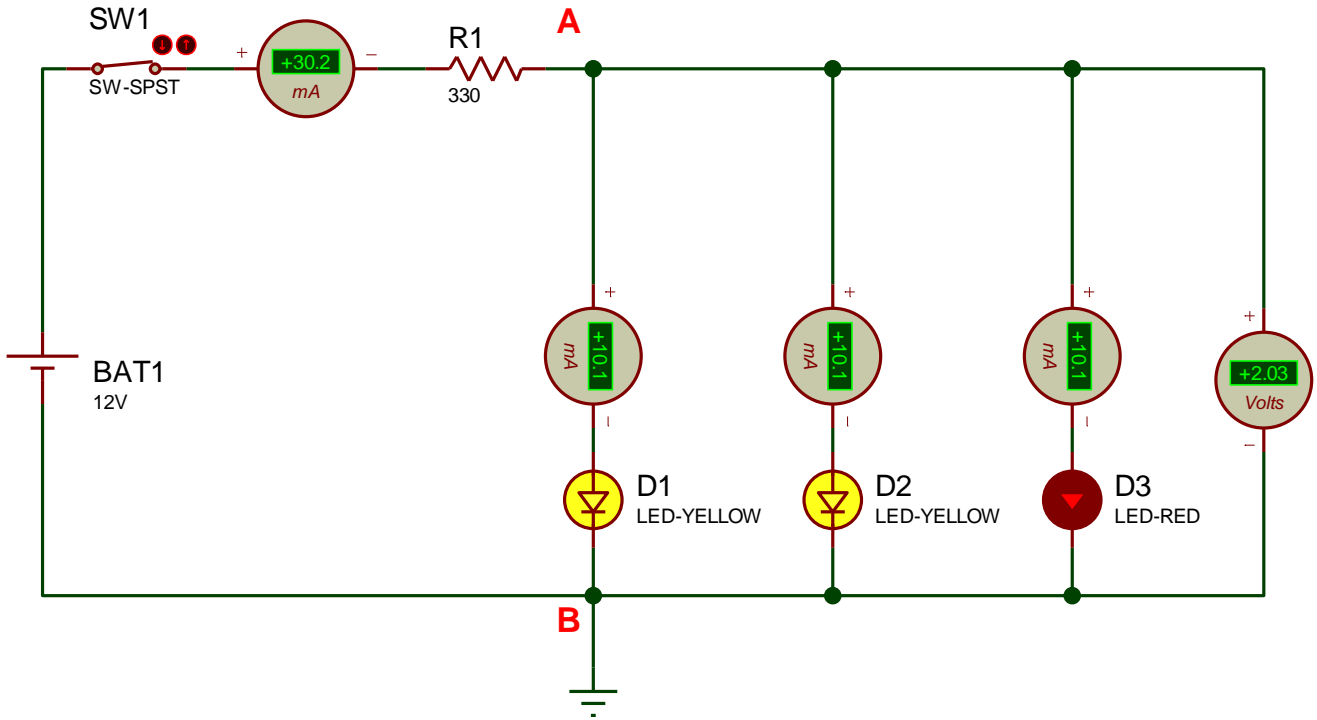


b)

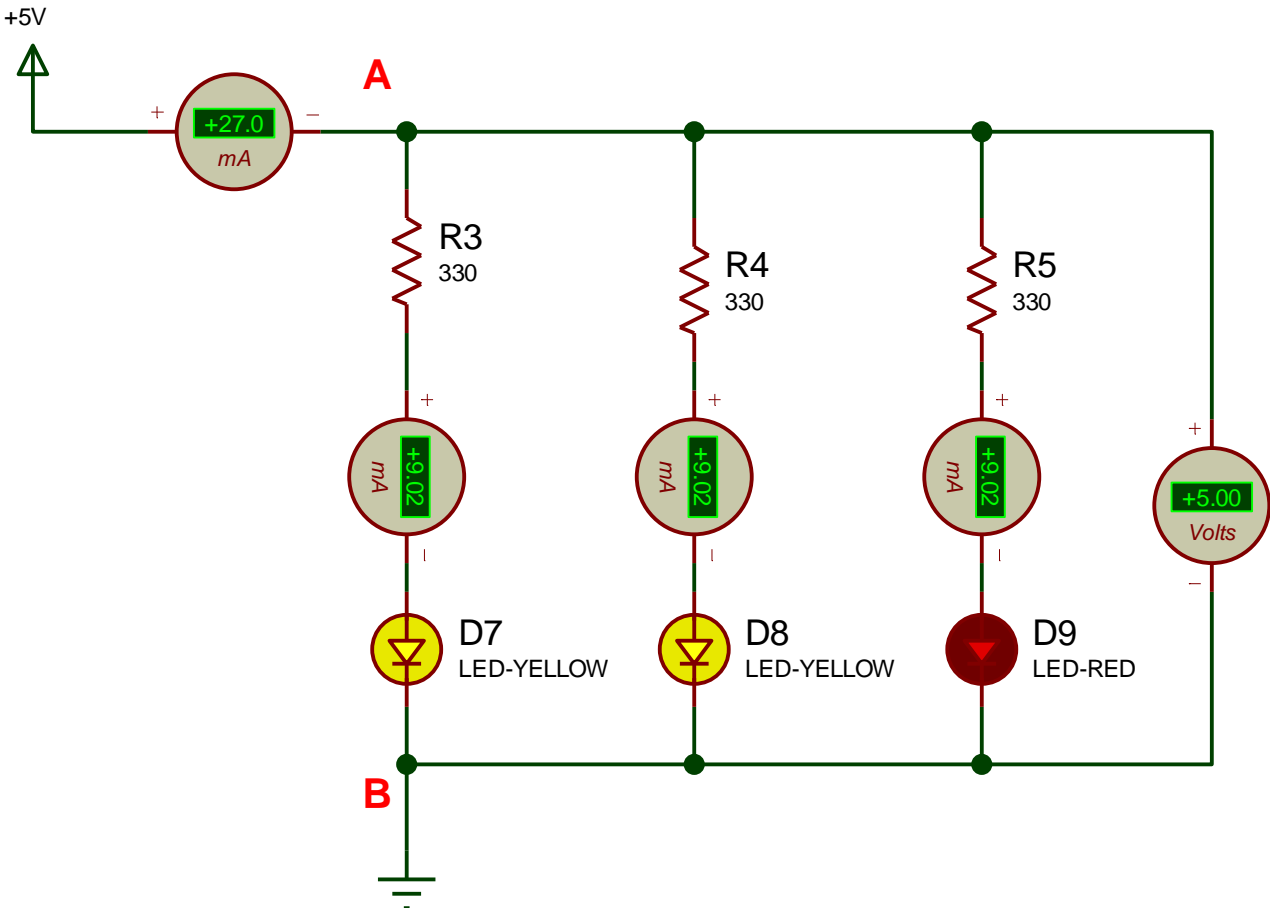

11. ACCENSIONE 3 LED IN SERIE

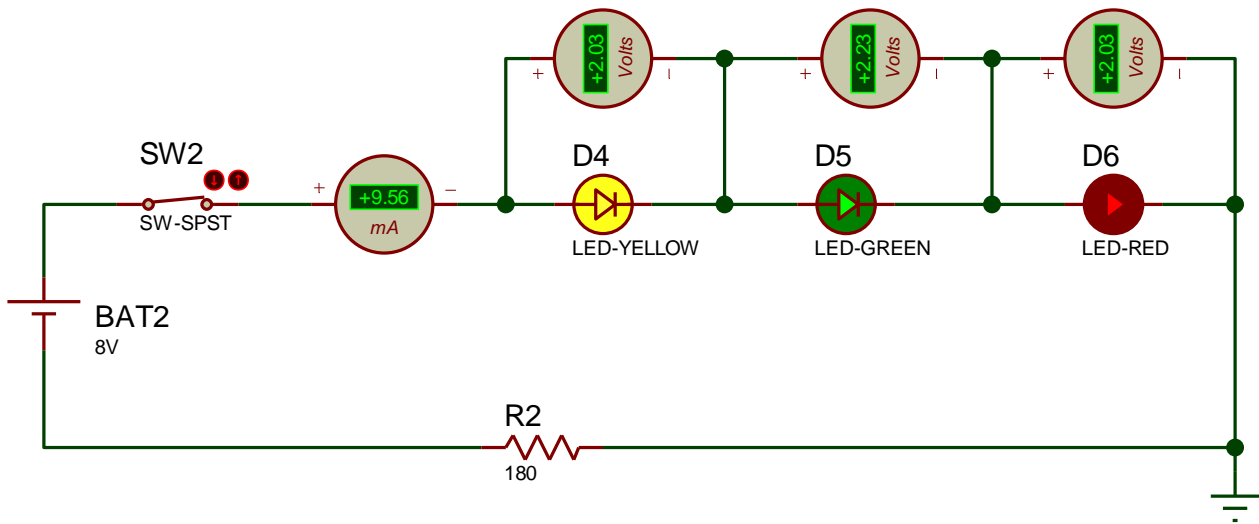

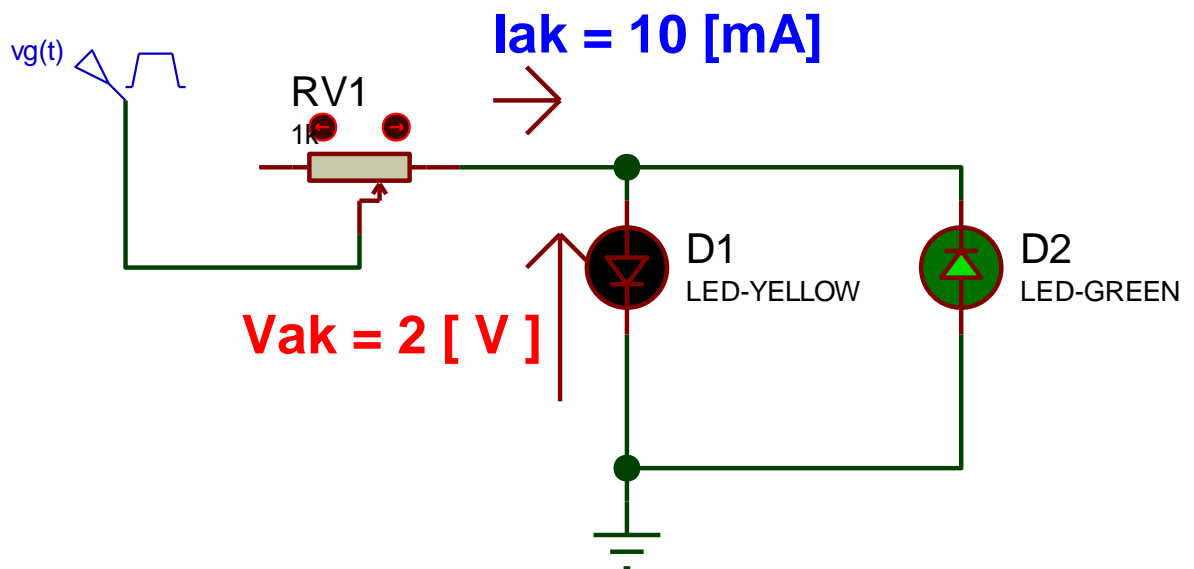12. ACCENSIONE 2 LED IN CONTROFASE , CON ONDA QUADRA



$$R = V_R / I_{ak} = (V_g - V_{ak}) / I_{ak} = (5 - 2) / 10 = 3 / 10 = 0,3 \text{ K} \gg 330 \text{ [Ohm]}$$